

Problem Set (8)

Resonance

- Measurements on a practical inductor at 10MHz give $L = 8 \text{ mH}$ and $Q_{\text{ind}} = 40$.
(a) Find the ideal capacitance C for parallel resonance at 10MHz and calculate the corresponding bandwidth β .
- Compare the resonant frequency of the circuit shown in Fig. 1 for $R = 0$ to that for $R = 50 \text{ ohm}$.

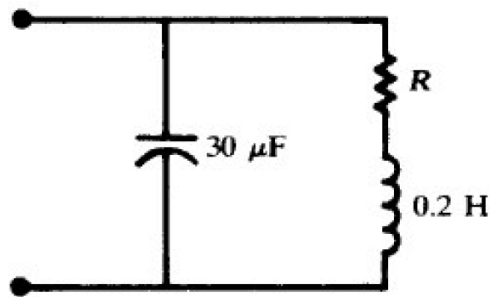


Figure 1

- A $20\text{-}\mu\text{F}$ capacitor is in parallel with a practical inductor represented by $L = 1 \text{ mH}$ in series with $R = 7 \Omega$. Find the resonant frequency, in rad/s and in Hz, of the parallel circuit.

“Ans: 1000 rad/s, 159.2 Hz”

- What must be the relationship between the values of R_L and R_C if the network shown in Fig. 2 is to be resonant at all frequencies?

“Ans: $R_L = R_C = 5 \Omega$.”

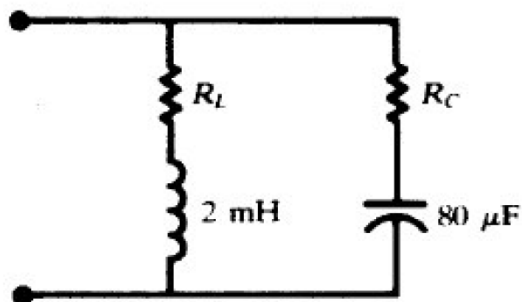


Figure 2

5. For the parallel network shown in Fig. 3, find the value of R for resonance; what is the value of X_c at resonance.

Ans. (a) 6.0Ω ; (b) $R_p = 6.67 \Omega$, $X_{C_p} = 20 \Omega$

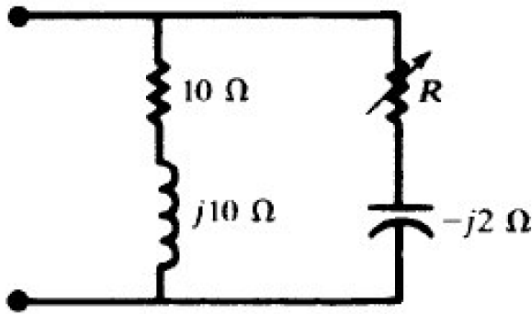


Figure 3

6. Assume that a sinusoidal voltage source with a variable frequency and $V_{\max} = 50 \text{ V}$ is applied to the circuit shown in Fig. 4.

(a) At what frequency f is $|I|$ a minimum?

(b) Calculate this minimum current.

(c) What is $|I_C|$ at this frequency?

Ans. (a) 2.05 kHz ; (b) 2.78 mA ; (c) 10.8 mA

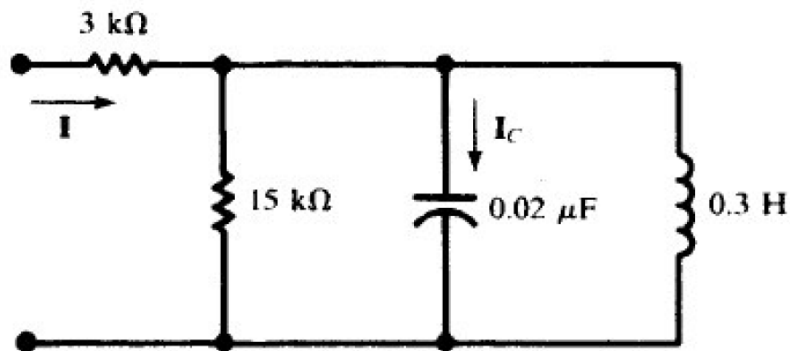


Figure 4

7. For the network of Fig. 5
- Find the resonance frequency..
 - Calculate the magnitude of V_C at resonance.
 - Determine the power absorbed at resonance.
 - Find the BW.

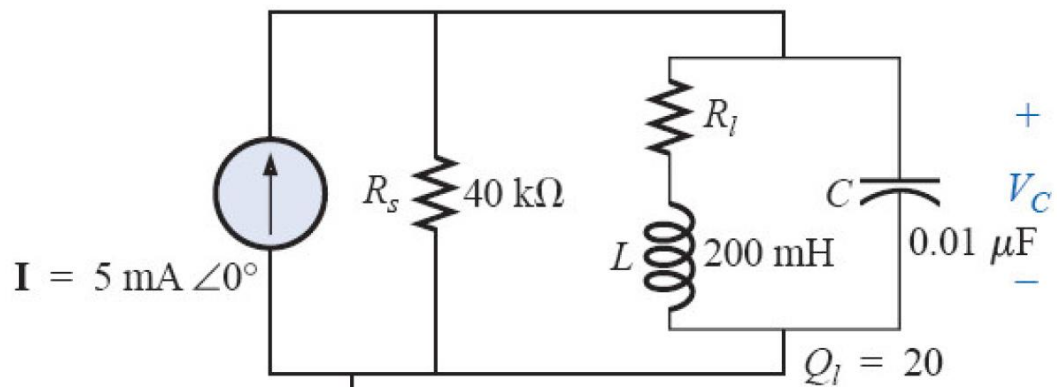


Figure 5

8. For the network of Fig. 6:
- Find the value of X_C at resonance .
 - Find the total impedance Z_{Tp} at resonance.
 - Find the currents I_L and I_C at resonance .
 - If the resonant frequency is 20,000 Hz, find the value of L and C at resonance.
 - Find the BW.

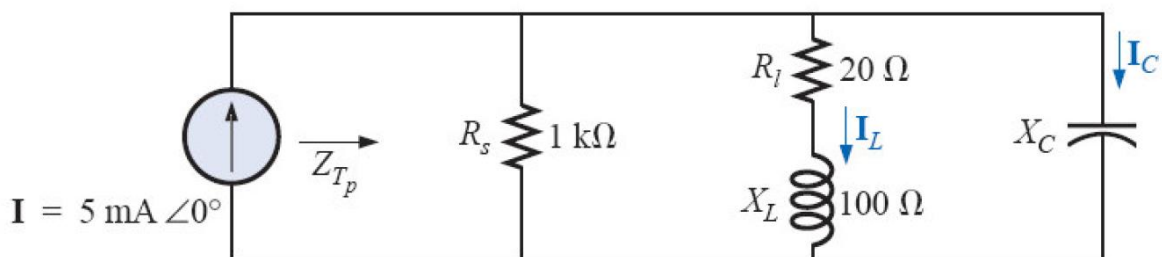


Figure 6