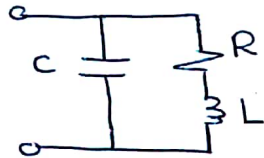


## Sheet 8

1] Measurements on a practical inductor at 10 MHz give  $L = 8 \text{ mH}$  and  $Q_{\text{ind}} = 40$

(a) Find the ideal capacitance  $C$  for parallel resonance at 10 MHz and calculate the corresponding bandwidth  $\beta$ .


Sol.



$$Q_{\text{ind}} = \frac{\omega_0 L}{R}$$

$$\therefore R = \frac{\omega_0 L}{Q_{\text{ind}}} = \frac{2\pi(10 \times 10^6)(8 \times 10^{-3})}{40} = 12566.37061 \, \Omega$$

For parallel resonance

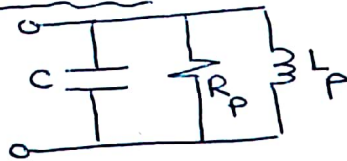

$$Y_{\text{series}} = Y_{\text{parallel}}$$

$$\frac{1}{R + j\omega L} = \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

$$\frac{(R - j\omega L)}{(R + j\omega L)(R - j\omega L)} = \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

$$\therefore \frac{R - j\omega L}{R^2 + (\omega L)^2} = \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

$$\therefore \frac{R}{R^2 + (\omega L)^2} - \frac{j\omega L}{R^2 + (\omega L)^2} = \frac{1}{R_p} - \frac{j}{\omega L_p}$$

$$\therefore R_p = \frac{R^2 + (\omega L)^2}{R}$$

$$\omega L_p = \frac{R^2 + (\omega L)^2}{\omega L}$$

$$X_c = X_{L_p} = \omega_0 L_p$$

$$\therefore X_c = 502968.9838$$

$$\therefore \frac{1}{\omega_0 C} = 502968.9838$$


$$\therefore C = 3.164 \times 10^{-14} \text{ F}$$

$$B\omega = \frac{1}{R_p C}$$

$$R_p = 20118759.36$$

$$\therefore B\omega = 1.571 \text{ M rad/Sec}$$

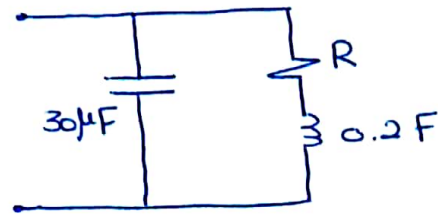2] Compare the resonant frequency of the circuit shown in Fig. 1 for  $R=0$  to that for  $R=50 \text{ ohm}$



Sol.

①  $R=0$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 30 \times 10^{-6}}} = 408.248 \text{ rad/Sec}$$

②  $R=50 \Omega$

For resonance:  $\text{imag}(Y_{eq}) = 0$

$$\therefore \frac{1}{R + j\omega l} + j\omega c = Y_{eq}$$

$$\begin{aligned} \therefore Y_{eq} &= \frac{R - j\omega l}{(R + j\omega l)(R - j\omega l)} + j\omega c \\ &= \frac{R - j\omega l}{R^2 + (\omega l)^2} + j\omega c \end{aligned}$$

$$\text{imag}(Y_{eq}) = \frac{-\omega_0 l}{R^2 + (\omega_0 l)^2} + \omega_0 c = 0$$

$$\therefore c = \frac{l}{R^2 + \omega_0^2 l^2}$$


$$l = R^2 c + \omega_0^2 l^2 c$$

$$\therefore l - R^2 c = \omega_0^2 l^2 c$$

$$\therefore \omega_0 = \sqrt{\frac{l - R^2 c}{l^2 c}} = \sqrt{\frac{0.2 - (50)^2 (30 \times 10^{-6})}{(0.2)^2 (30 \times 10^{-6})}} = 322.75 \text{ rad/Sec}$$

3] A  $20\mu\text{F}$  capacitor is in parallel with a practical inductor represented by  $L = 1\text{mH}$  in series with  $R = 7\Omega$ . Find the resonant freq. in rad/sec and in Hz of the parallel circuit.

Sol.

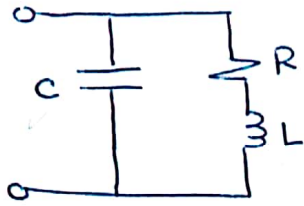

For resonance

$$\text{imag.}(Y_{eq}) = 0$$

$$\therefore Y_{eq} = j\omega C + \frac{1}{R + j\omega L}$$

$$\therefore Y_{eq} = j\omega C + \frac{(R - j\omega L)}{(R + j\omega L)(R - j\omega L)}$$

$$\therefore Y_{eq} = j\omega C + \frac{R - j\omega L}{R^2 + (\omega L)^2}$$

$$\therefore \text{imag}(Y_{eq}) = \omega_0 C - \frac{\omega_0 L}{R^2 + (\omega_0 L)^2} = 0$$

$$\therefore C = \frac{L}{R^2 + (\omega_0 L)^2}$$


$$\therefore CR^2 + \omega_0^2 L^2 C = L$$

$$\therefore \omega_0 = \sqrt{\frac{L - CR^2}{L^2 C}} = \sqrt{\frac{(1 \times 10^{-3}) - (20 \times 10^{-6} \times 7^2)}{(1 \times 10^{-3})^2 (20 \times 10^{-6})}}$$

$$\omega_0 = 1000 \text{ rad/sec}$$

$$f_0 = \frac{\omega_0}{2\pi} = 159.155 \text{ Hz}$$

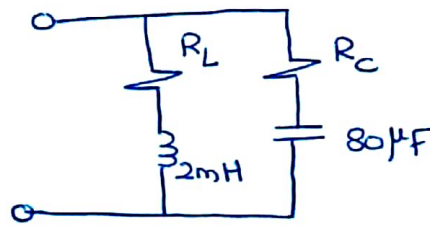4] what must be the relationship between the values of  $R_L$  and  $R_C$  if the network shown in Fig. 2 is to be resonant at all frequencies?



Sol.

@ resonance :  $\text{imag}(Y_{eq}) = 0$

$$\therefore Y_{eq} = \frac{1}{R_L + j\omega L} + \frac{1}{R_C + \frac{1}{j\omega C}}$$

$$\therefore Y_{eq} = \frac{1}{R_L + j\omega L} + \frac{j\omega C}{j\omega C R_C + 1}$$

$$\therefore Y_{eq} = \frac{R_L - j\omega L}{R_L^2 + (\omega L)^2} + \frac{j\omega C(1 - j\omega C R_C)}{1 + (\omega C R_C)^2}$$

$$\therefore Y_{eq} = \frac{R_L - j\omega L}{R_L^2 + (\omega L)^2} + \frac{j\omega C + \omega^2 C^2 R_C}{1 + (\omega C R_C)^2}$$

$$\therefore \text{imag}(Y_{eq}) = \frac{-\omega L}{R_L^2 + (\omega L)^2} + \frac{\omega C}{1 + (\omega C R_C)^2} = 0$$

$$\therefore \frac{L}{R_L^2 + (\omega_0 L)^2} = \frac{C}{1 + (\omega_0 C R_C)^2}$$

$$\therefore L + L\omega_0^2 C^2 R_C^2 = C R_L^2 + C\omega_0^2 L^2$$

$$\therefore \boxed{LC^2 R_C^2 = CL^2} \quad \& \quad \boxed{L = CR_L^2} \rightarrow (2)$$

From eq. 1

$$\therefore R_C = \sqrt{\frac{L}{C}}$$

$$= 5\Omega$$


From eq. 2

$$R_L = \sqrt{\frac{L}{C}} = 5\Omega$$

$$\therefore \boxed{R_L = R_C = 5\Omega}$$



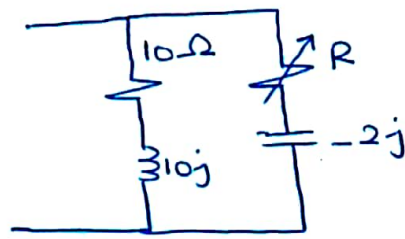- 5] For the parallel network shown in Fig. 3, find the value of  $R$  for resonance, what is the value of  $X_L$  at resonance.



Sol.

@ resonance :

$$\text{imag.}(Y_{eq}) = 0$$

$$\therefore Y_{eq} = \frac{1}{10 + 10j} + \frac{1}{R - 2j}$$

$$\therefore Y_{eq} = \frac{10 - 10j}{100 + 100} + \frac{R + 2j}{R^2 + 4}$$


$$\therefore \text{imag}(Y_{eq}) = \frac{-10}{200} + \frac{2}{R^2 + 4} = 0$$

$$\therefore \frac{10}{200} = \frac{2}{R^2 + 4}$$

$$\therefore R^2 + 4 = \frac{2(200)}{10} = 40$$

$$\therefore R^2 = 36 \Rightarrow \therefore R = 6 \Omega$$

To get  $X_C$  at resonance

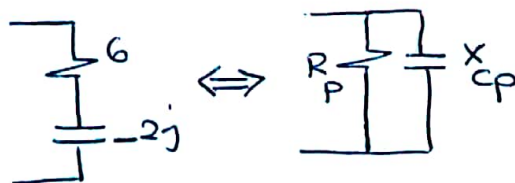

$$Y_{\text{series}} = Y_{\text{parallel}}$$

$$\therefore \frac{1}{6 - 2j} = \frac{1}{R_P} + j\omega C_P \Rightarrow \therefore \frac{6 + 2j}{36 + 4} = \frac{1}{R_P} + j\omega C_P$$

$$\therefore \frac{1}{R_P} = \frac{6}{40} \Rightarrow R_P = 6.67 \Omega$$

$$\omega C_P = \frac{2}{40}$$


$$\therefore X_{CP} = \frac{1}{\omega C_P} \Rightarrow X_{CP} = 20 \Omega$$

6] Assume that a sinusoidal voltage source with a variable frequency and  $V_{\max} = 50\text{ V}$  is applied to the circuit shown in Fig. 4

(a) At what frequency  $f$  is  $|I|$  a minimum?

(b) Calculate this minimum current

(c) what is  $|I_c|$  at this frequency?

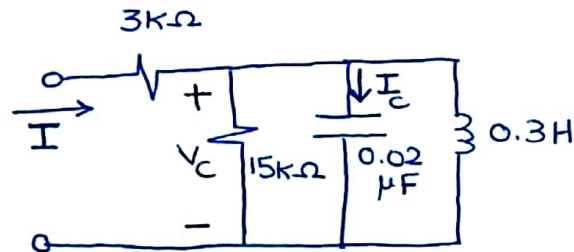

Sol.

$$(a) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.3 \times 0.02 \times 10^{-6}}} = 12909.94 \text{ rad/Sec}$$

$$\therefore f_0 = \frac{\omega_0}{2\pi} = 2054.68 \text{ Hz}$$

$$(b) |I|_{\min} = \frac{V_{\max}}{(3k + 15k)} = \frac{50}{18k} = 2.78 \times 10^{-3} \text{ A}$$

$$(c) I_c = \frac{V_c}{\frac{1}{j\omega C}} = V_c j\omega C$$

$$\therefore |I_c| = |V_c| \omega C$$


$$\therefore V_c = I_{\min} \times 15000$$

$$\therefore |V_c| = |I_{\min}| \times 15000 = 41.67 \text{ V}$$

$$\therefore |I_c| = 41.67 \times 12909.94 \times 0.02 \times 10^{-6} = 0.0108 \text{ A} = 10.8 \text{ mA}$$

7] For the network of fig. 5

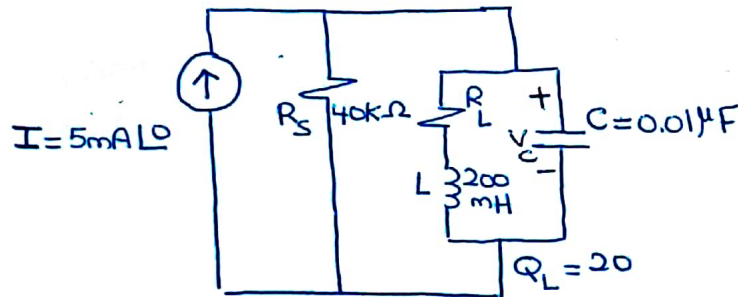- Find the resonance frequency
- Calculate the magnitude of  $V_C$  at resonance
- Determine the power absorbed at resonance
- Find the BW.




Sol.

$$(a) \because Q_L = \frac{\omega_0 L}{R_L}$$

$$\therefore 20 = \frac{\omega_0 \times 200 \times 10^{-3}}{R_L}$$
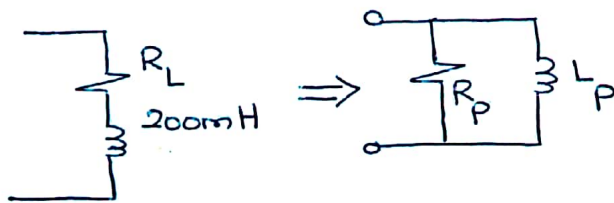
$$\therefore \omega_0 = \frac{20 R_L}{200 \times 10^{-3}} = 100 R_L \rightarrow (3)$$



$$X_{L_P} = \frac{R_L^2 + (X_L)^2}{X_L} \text{ "as proved in question 1"}$$

$$\therefore X_{L_P} = X_C \text{ (at resonance)}$$

$$\therefore X_{L_P} = \frac{1}{\omega_0 C} = \frac{1}{\omega_0 \times 0.01 \times 10^{-6}} \rightarrow (2)$$

From 1 & 2

$$\therefore \frac{1}{\omega_0 \times 0.01 \times 10^{-6}} = \frac{(R_L)^2 + (\omega_0 L)^2}{\omega_0 L}$$

using eq. 3

$$\therefore \frac{1}{0.01 \times 10^{-6}} = \frac{R_L^2 + (100 R_L \times 200 \times 10^{-3})^2}{200 \times 10^{-3}}$$

$$\therefore R_L^2 + 400 R_L^2 = 2 \times 10^7$$


$$\therefore R_L^2 (1 + 400) = 2 \times 10^7$$

$$\therefore R_L = 223.328 \Omega$$

From eq. 3:  $\omega_0 = 22332.8 \text{ rad/Sec}$

$$f_0 = 3554.376 \text{ Hz}$$

(b)

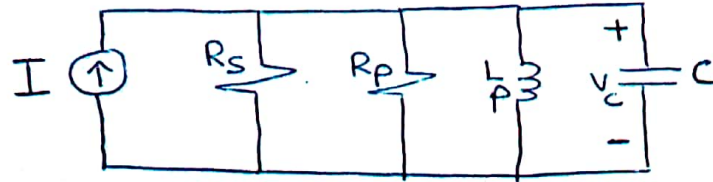

$$\therefore R_p = \frac{R_L^2 + (\omega_0 L)^2}{R_L}$$

$$\therefore R_p = \frac{(223.328)^2 + (22332.8 \times 200 \times 10^{-3})^2}{223.328}$$

$$R_p = 89554.528 \, \Omega$$

$$R_s \parallel R_p \Rightarrow R_{eq} = \frac{R_s R_p}{R_s + R_p} = 27649.988 \, \Omega$$

@ resonance:  $V_c = I R_{eq}$

$$\therefore |V_c| = |I| R_{eq} = 5 \times 10^{-3} \times 27649.988$$

$$|V_c| = 138.25 \, V$$

$$(c) \, P = |I|^2 R_{eq} = (5 \times 10^{-3})^2 \times 27649.988$$


$$P = 0.69 \, W$$

$$(d) \, BW = \frac{1}{R_{eq} C} = \frac{1}{27649.988 \times 0.01 \times 10^{-6}} = 3616.638 \, \text{rad/sec}$$



8] For the network of Fig. 6:

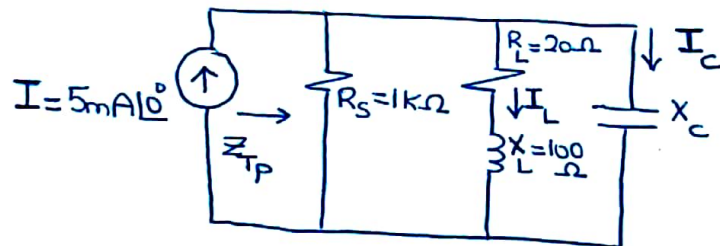- Find the value of  $X_C$  at resonance
- Find the total impedance  $Z_{TP}$  at resonance
- Find the currents  $I_L$  and  $I_C$  at resonance
- If the resonant frequency is 20,000 Hz, find the value of  $L$  and  $C$  at resonance
- Find the BW.




Sol.

(a) @ resonance:  $X_C = X_{LP}$

$$\therefore X_{LP} = \frac{R_L^2 + (X_L)^2}{X_L} \text{ "as proved in question 1"}$$

$$\therefore X_{LP} = \frac{(20)^2 + (100)^2}{100} = 104 \Omega$$

$$\therefore X_C = 104 \Omega$$

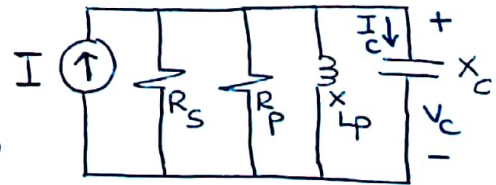

(b)  $Z_{TP}$  at resonance  $\Rightarrow R_S \parallel R_P$

$$\therefore R_P = \frac{R_L^2 + X_L^2}{R_L}$$

$$\therefore R_P = \frac{(20)^2 + (100)^2}{20} = 520 \Omega$$

$$Z_{TP} = R_{eq} = \frac{R_S R_P}{R_S + R_P} = \frac{1 \times 10^3 \times 520}{10^3 + 520} = 342.11 \Omega$$

(c) @ resonance:  $V_c = I R_{eq}$   
 $\therefore V_c = 5 \times 10^{-3} \times 342.11$   
 $= 1.71055 \text{ V.}$

$\therefore I_c = \frac{V_c}{-jX_c} \Rightarrow \therefore I_c = \frac{1.71055}{-j104} \Rightarrow I_c = 0.016j \text{ A}$

$\therefore I_L = \frac{V_c}{20 + 100j} = \frac{1.71055}{20 + 100j} = 0.0168 \angle -78.69^\circ \text{ A}$

(d)  $f_0 = 20,000 \Rightarrow \omega_0 = 2\pi f_0 = 125663.7061 \text{ rad/Sec}$

$\therefore X_c = \frac{1}{\omega_0 C} = 104$

$\therefore C = \frac{1}{104 \omega_0} = 7.652 \times 10^{-8} \text{ F}$

$\therefore X_L = \omega_0 L = 100$

$\therefore L = \frac{100}{\omega_0} = 7.958 \times 10^{-4} \text{ H}$

(e)  $BW = \frac{1}{R_{eq} C} = \frac{1}{(342.11 \times 7.652 \times 10^{-8})}$   
 $= 38199.64 \text{ rad/Sec}$